



# INTRODUCTION TO ELECTICAL AND ELECTRONICS ENGINEERING

---

SUBMITTED BY GROUP 5

MEENAKSHY S (CB.EN.U4AIE22032)

NAGA KOUSHIK (CB.EN.U4AIE22046)

VISHRUT SAWARNYA (CB.EN.U4AIE22059)

SUBHASHINI SUDHAKAR (CB.EN.U4AIE22061)

# INTRODUCTION

---

- Optocouplers, also known as optoisolators, are crucial for achieving electrical isolation in electronic systems.
- They use optical communication to transmit signals while maintaining separation. In this activity, we will construct an optocoupler using an infrared (IR) LED and an NPN phototransistor.
- This optical link enables communication between circuits while keeping them electrically isolated. We will also explore the operation of integrated optocouplers for analog signal isolation and current regulation.
- Through this activity, participants will gain hands-on experience and expand their knowledge in electronic circuit design and implementation.

# Uses of optocouplers

---

- Optocouplers are used for electrical isolation in various applications.
- They protect components from voltage spikes and transients.
- Optocouplers ensure reliable signal transmission and data integrity.
- They find applications in power electronics, industrial control systems, and automotive electronics.
- Optocouplers are used in medical devices, audio equipment, and power supply designs.
- They provide isolation in aerospace, military, and renewable energy systems.
- Optocouplers are employed in motor control circuits for precise control and protection.

# Advantages of optocoupler

---

- Electrical isolation: Optocouplers provide effective electrical isolation, safeguarding components from voltage spikes and damage.
- Noise immunity: Optocouplers eliminate noise and interference, ensuring reliable signal transmission.
- Signal integrity: Optocouplers maintain signal integrity, reducing distortion and improving system performance.
- Compact and versatile: Optocouplers are adaptable to different applications and can be integrated into compact designs.
- Wide voltage range: Optocouplers can handle high voltages and voltage transients, offering flexibility in various scenarios.
- Low power consumption: Optocouplers consume minimal power, making them energy-efficient.
- Easy integration: Optocouplers can be easily integrated into existing circuits without extensive modifications.
- Safety: Optocouplers provide galvanic isolation, enhancing safety and protecting sensitive equipment.

# Disadvantages of optocoupler

---

- Limited bandwidth: Optocouplers have a limited bandwidth for high-speed applications.
- Temperature sensitivity: Optocouplers can be sensitive to temperature variations.
- Aging and degradation: Optocouplers may experience reduced performance and reliability over time.
- Response time: Optocouplers have a finite response time, introducing potential delays.
- Size and cost: Optocouplers can be larger and more costly compared to alternative solutions.
- Compatibility limitations: Optocouplers may have limitations with voltage or signal levels.
- Sensitivity to ambient light: Optocouplers can be susceptible to interference from ambient light.

# Material required

---

- a. ADALM2000 Active Learning Module**
- b. Solder-less breadboard,**
- c. jumper wire kit**
- d. 2 2.2 k $\Omega$  resistors**
- e. 1 OP27 operational amplifier**
- f. 2 QSD123 LED lights**


# The NPN transistor Optocoupler Background

---

- Optocouplers transfer electrical signals using light across an isolation barrier
  - .- They protect components from high voltages and voltage spikes.- Input-to-output voltages range from 3kV to 10kV.
- Optocouplers can withstand fast voltage transients up to 10kV/ $\mu$ s
  - .- They consist of an infrared LED as the input and a photo-detector on the output side
  - .- An isolation barrier separates the input and output sections.- When the LED is off, no light is emitted, and the photo-detector remains off
  - .- When the LED is on and emits light, the photo-detector turns on if sufficient photo current is received
  - .- Optocouplers ensure signal transmission while preventing damage and interference.

# Figure of NPN transistor Optocoupler

---

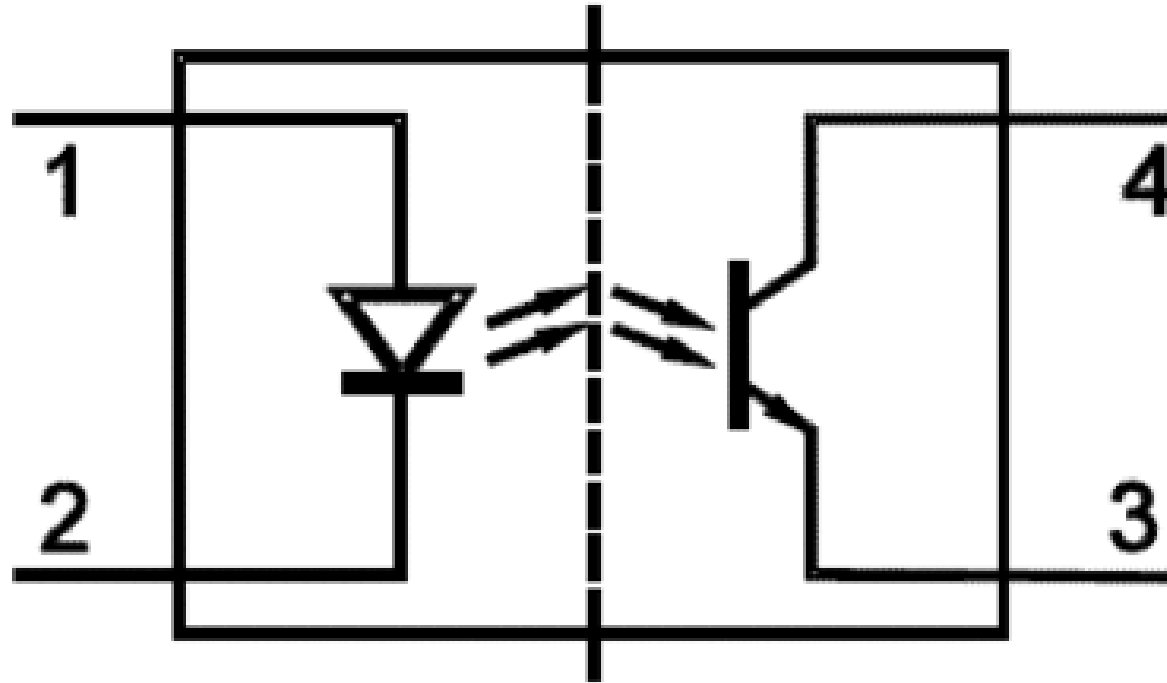



# Construction Directions

---


- The first step of this activity is to construct an optocoupler using an infrared LED and NPN phototransistor.
- The components required for this construction are provided in the ADALP2000 Analog Parts Kit
- .- If the ADALP2000 Analog Parts Kit is not available, similar devices can be used as substitutes, but the results may vary based on the components used.

QED-123 Infrared LED




QSD123 Infrared Transistor

- Bend the leads of the LED and phototransistor 90 degrees to ensure they face each other and are at the same level when inserted into the solder-less breadboard.
- Use a short length of tubing or black electrical tape, cut to the appropriate width, to wrap around the combined LED and phototransistor.
- This alignment and covering method helps maintain proper alignment, prevent stray ambient light, and ensure optimal performance.

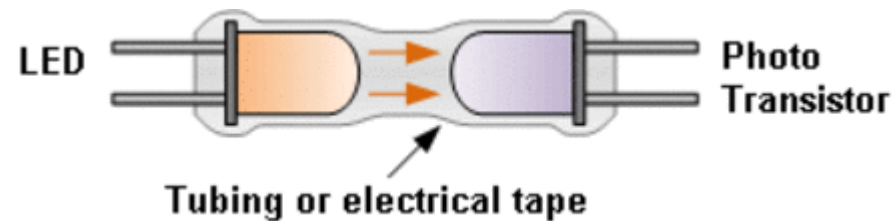

# Circuit diagram


---

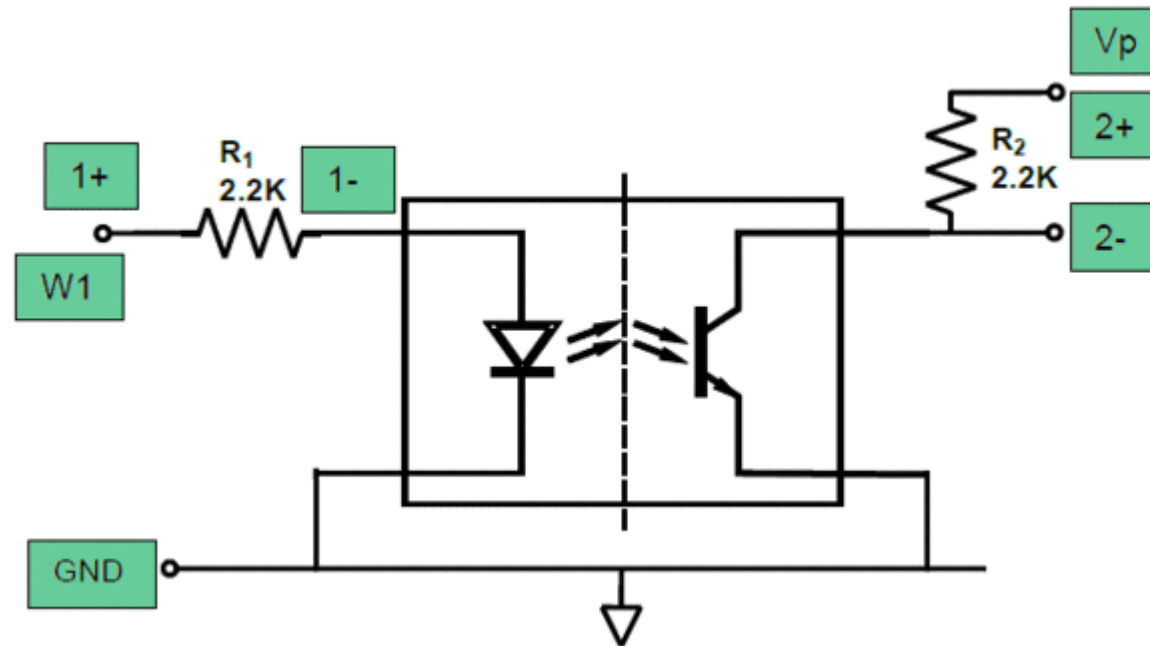

Optocoupler Input to Output characteristics


# Hardware Setup

---

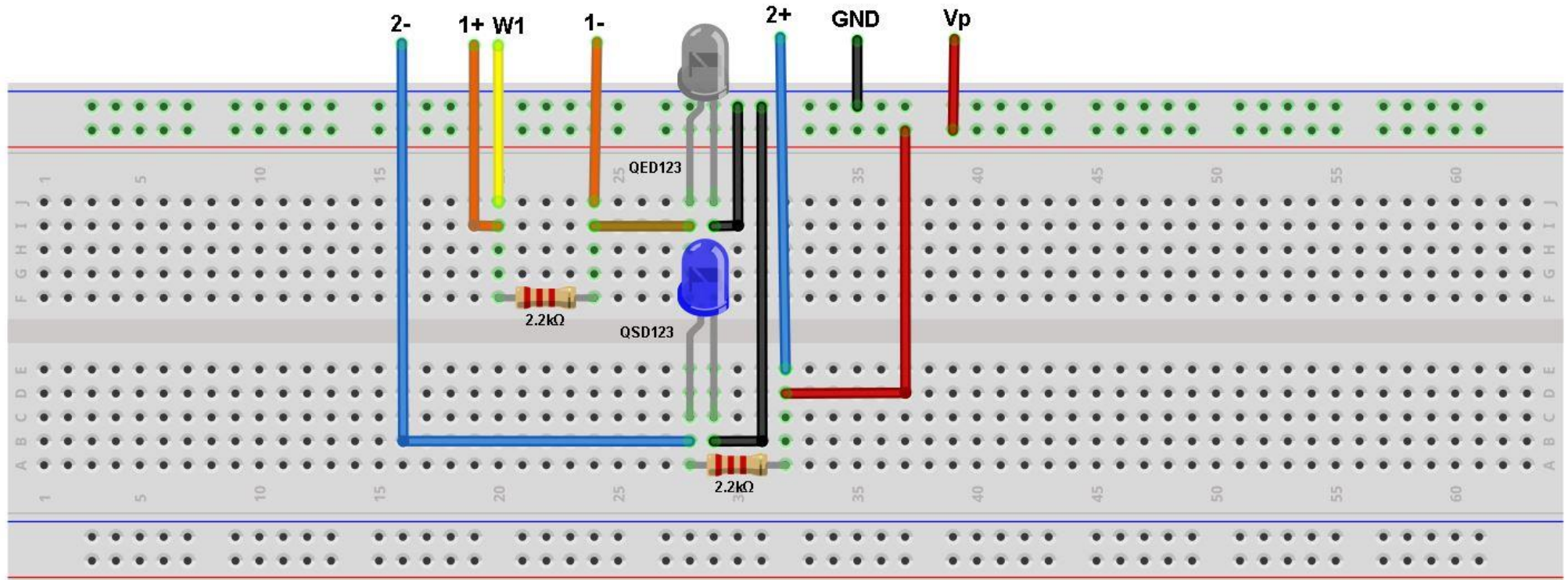

# Result

---

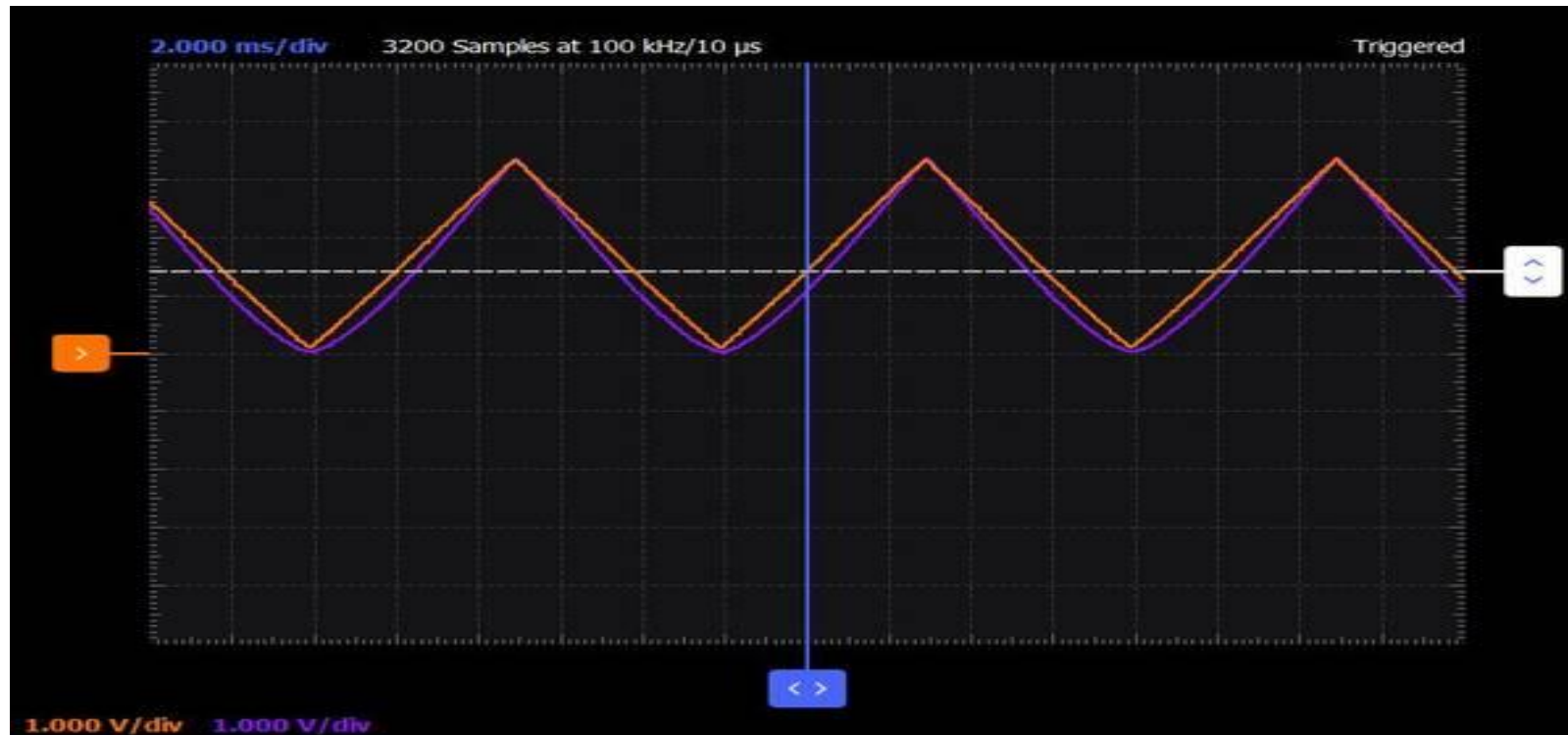

# Contributions

---

- Meenakshy (CB.EN.U4AIE22032 ): About Optocouplers
- Naga Koushik (CB.EN.U4AIE22046) : Hardware setup
- Vishrut sawarnya (CB.EN.U4AIE22059) : Hardware setup
- Subhashini (CB.EN.U4AIE22061) : Circuit diagram